



Suez University
Faculty of Petroleum and Mining Engineering
BSE225, Spring Term 16-17



Binary Logic

Lecture 4 – Monday March 13, 2017

Outline


- Boolean Logic
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- Logic Circuits
- Summary

Outline

- **Boolean Logic**
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- Logic Circuits
- Summary

Boolean Logic

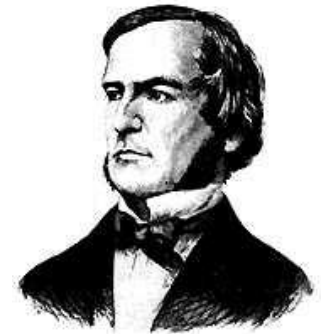- Boolean logic is a branch of mathematics that deals with rules for manipulating two logical values **true** and **false**.
- It was named after George Boole.
- Boolean logic is simply a way of comparing individual bits.
- Why is Boolean logic so relevant to computers?



George Boole (1815-1864)
British mathematician
and philosopher




- Straightforward mapping to binary digits!
- Binary digit values can be thought of as:
ON/OFF, High/Low, Yes/No, 1/0

Outline

- Boolean Logic
- **Boolean Algebra**
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- Logic Circuits
- Summary

Boolean Algebra

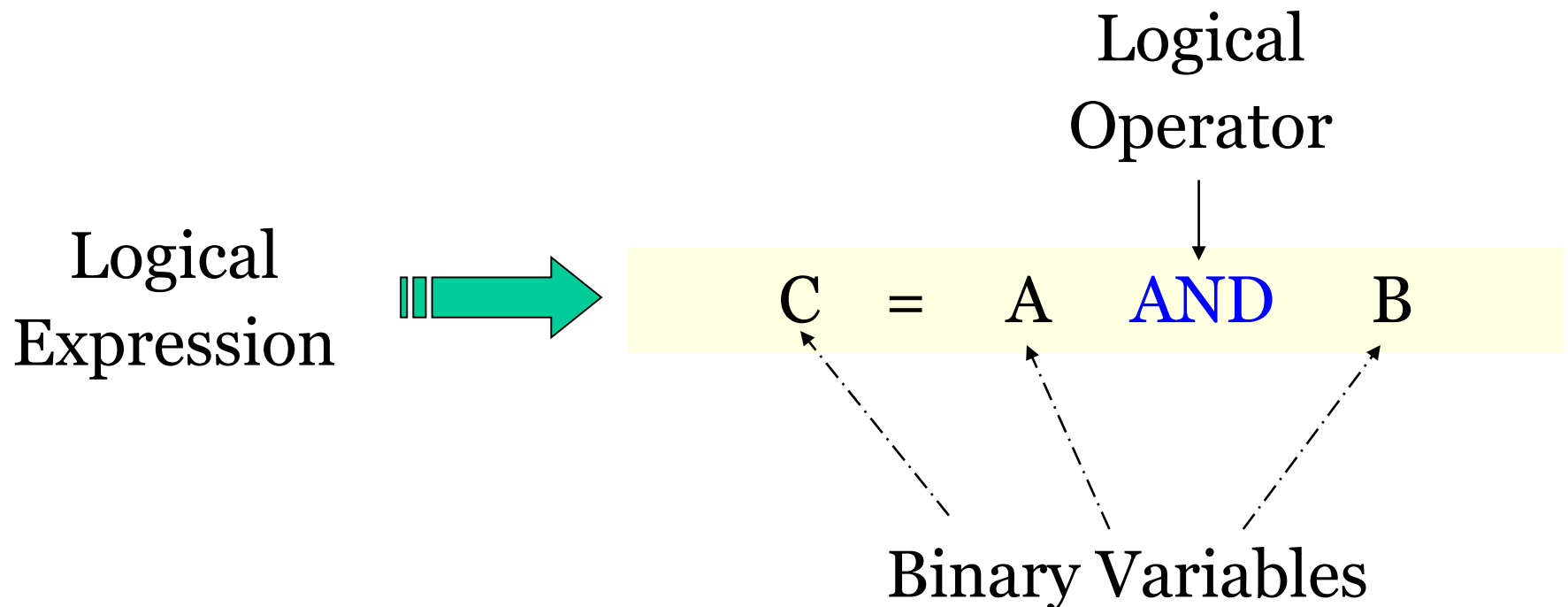- An algebra in which elements have one of two values and the algebraic operations defined on the set are logical OR, a type of addition, and logical AND, a type of multiplication.




Outline

- Boolean Logic
- Boolean Algebra
- **Binary Variables**
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- Logic Circuits
- Summary

Binary Variables

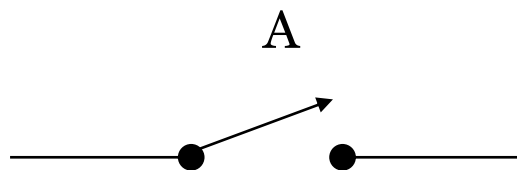
- Binary variables take on one of two values, **true** or **false**.
- Variable identifiers: A, B, C, X, Y,



A = false

OFF

0

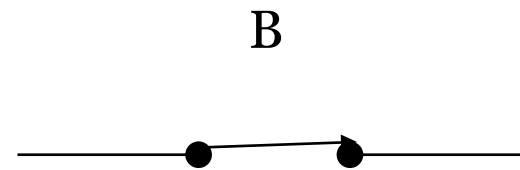

B = true

ON

1

Outline


- Boolean Logic
- Boolean Algebra
- Binary Variables
- **Binary Operators**
 - **Logical AND**
 - **Logical OR**
 - **Logical Negation**
- Boolean Expressions
- Logic Gates
- Logic Circuits
- Summary

Binary Operators

- Logical AND
- Logical OR
- Logical Negation (NOT).

Binary Operators: Logical AND

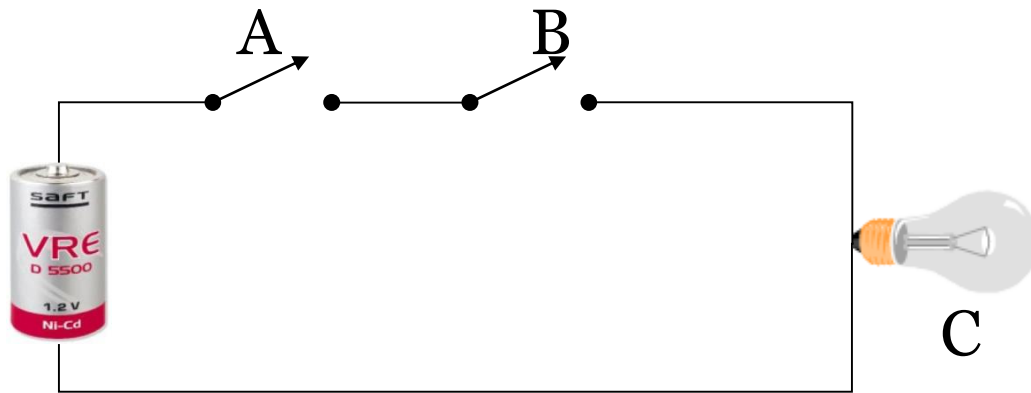- AND is denoted by a dot (\cdot)
- Consider two logic variables A and B and the result is C.
- C is true if and only if A is true **AND** B is true



In order for current to flow, both switches must be closed

$$C = A.B$$

Truth Table

Inputs		Output
A	B	$C=A.B$
0	0	0
0	1	0
1	0	0
1	1	1


Binary Operators: Logical AND

ON/OFF

Person Sensor

Alarm Switch

ON/OFF

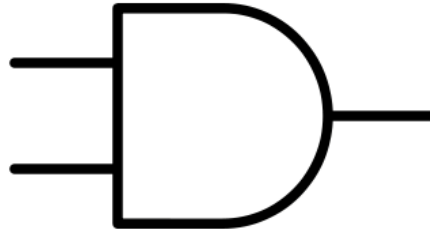

ON/OFF

Burglar Alarm

If both the Person Sensor **AND** the Alarm Switch are on then the Burglar Alarm is activated



Binary Operators: Logical AND

- $(A \text{ AND } B)$ yields true only if both A and B are true.


Example: Adult blood pressure is considered normal at 120/80 where the first number is the systolic pressure and the second is the diastolic pressure.

A = True if Systolic Pressure = 120


B = True if Diastolic Pressure = 80

C = True \Rightarrow Blood pressure is normal

C = A.B

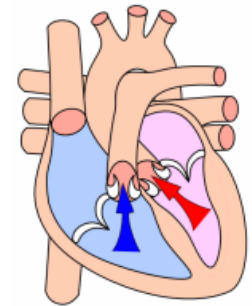


Systolic Pressure

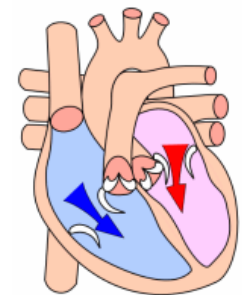

Diastolic Pressure

Binary Operators: Logical AND

- Example-2: Google Search

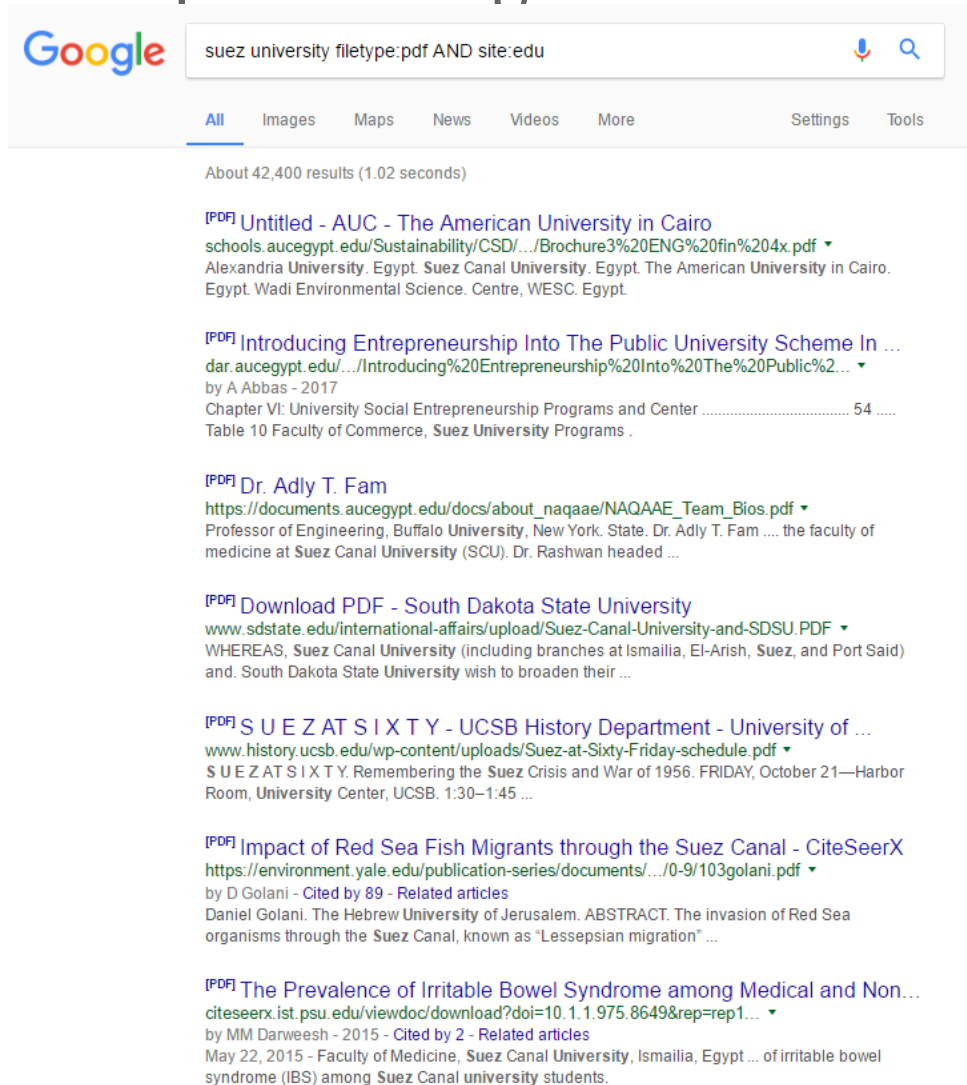

operator:parameter


filetype:pdf will search for pdf only.

site:edu will search all site in edu top domain.

suez university filetype:pdf AND site:edu will search for pdf and all site in edu top domain.

Binary Operators: Logical OR

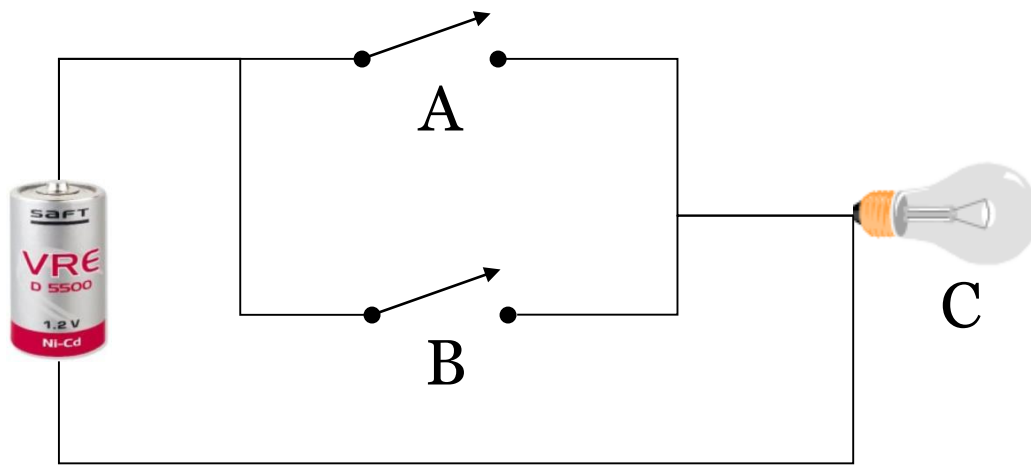- OR is denoted by a plus (+)
- Consider two logic variables A and B and the result is C.
- C is true if A is true **OR** B is true



Current flows if either switch is closed

$$C = A+B$$

Truth Table

Inputs		Output
A	B	$C = A+B$
0	0	0
0	1	1
1	0	1
1	1	1


Binary Operators: Logical OR

ON/OFF

Front Doorbell Switch

Back Doorbell Switch

ON/OFF

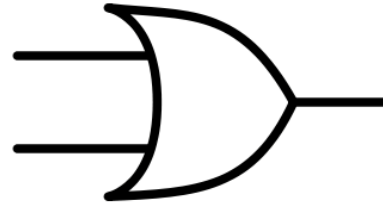

ON/OFF

Doorbell

If either the Front Doorbell Switch **OR** the Back Doorbell Switch is pressed then the Doorbell rings



Binary Operators: Logical OR

- $(A \text{ OR } B)$ yields true only if either A or B, or both are true.


Example: Adult blood pressure is considered normal at 120/80 where the first number is the systolic pressure and the second is the diastolic pressure.

A = True if Systolic Pressure \neq 120


B = True if Diastolic Pressure \neq 80

C = True \Rightarrow Blood pressure is abnormal

C = A+B

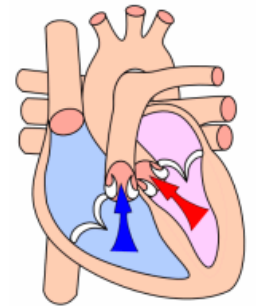

Systolic Pressure

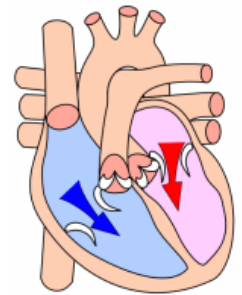

Diastolic Pressure

Binary Operators: Logical OR

- Example-2: Google Search

The screenshot shows a Google search interface with the query "suez university filetype:pdf OR site:edu". Below the search bar, there are tabs for "All", "Maps", "Images", "News", "Videos", "More", "Settings", and "Tools". The search results indicate "About 415,000 results (0.87 seconds)".

The first result is a map showing the location of "The British University In Egypt" and "Suez Canal University". Below the map, there are two entries:

- The British University In Egypt**
4.5 ★★★★★ (167) - University
19283
Closed now
WEBSITE DIRECTIONS
- Suez Canal University**
4.1 ★★★★★ (63) - University
Ismailia - 064 3200395
WEBSITE DIRECTIONS

Below the map, there are three search results:

- Suez University Faculty of petroleum & Mining Eng - Academia.edu**
suezuniv.academia.edu/
Academia.edu is a place to share and follow research.
- Suez Canal University | Suez University, Faculty of Education, D. of ...**
https://scuegypt.academia.edu/.../Suez_University.../Documents
Academia.edu is a place to share and follow research.
- ahmed bhran | Suez University Faculty of petroleum & Mining Eng ...**
suezuniv.academia.edu/ahmedbhran
ahmed bhran, Suez University Faculty of petroleum & Mining Eng, Refining and Petrochemical Engineering Department, Faculty Member. Studies Environmental ...
- Suez Canal University, Faculty of Medicine (Egypt) - VIVO**
vivo.med.cornell.edu/display/org-200001001
Suez Canal University, Faculty of Medicine (Egypt) University uri icon. ©2017 VIVO Project | Terms of Use | Powered by VIVO · About · Contact Us · Support.

operator:parameter


`filetype:pdf` will search for pdf only.

`site:edu` will search all site in edu top domain.

`suez university filetype:pdf OR site:edu` will search for pdf or all site in edu top domain.

Binary Operators: Logical Negation

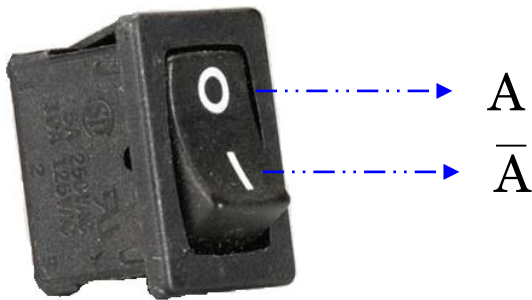
- NOT is denoted by a bar ($\bar{\quad}$) over, a single quote mark (') after, or \sim before the variable.
- Consider a logic variable A and the result is C.
- C is true if A is false and vice versa.
- $C = \bar{A}$ or $C = A'$ or $C = \sim A$



Truth Table

Input	Output
A	$C = \bar{A}$
0	1
1	0

Binary Operators: Logical Negation

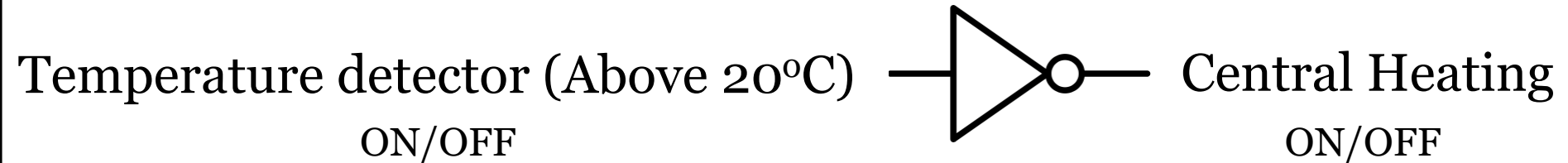

If the temperature is above 20°C then the Central Heating is switched off.

If the temperature is below 20°C then the Central Heating is switched on



Binary Operators: Logical Negation

- Inverts its operand.


Example: Adult blood pressure is considered normal at 120/80 where the first number is the systolic pressure and the second is the diastolic pressure.

$A = \text{True}$ if Systolic Pressure = 120


$\overline{A} = \text{False}$ \Rightarrow Systolic Pressure \neq 120

$B = \text{True}$ if Diastolic Pressure = 80

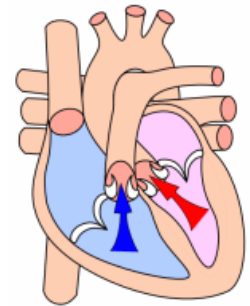$\overline{B} = \text{False}$ \Rightarrow Diastolic Pressure \neq 80



Systolic Pressure

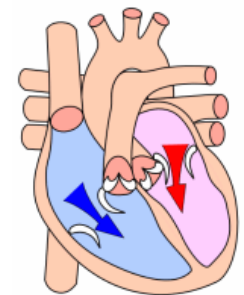

Diastolic Pressure

Logic Gates: NOT Gate

- Street Light

ON/OFF


Switch

Light sensor (LDR)

Bright=1, Dark=0

Street Light

ON/OFF

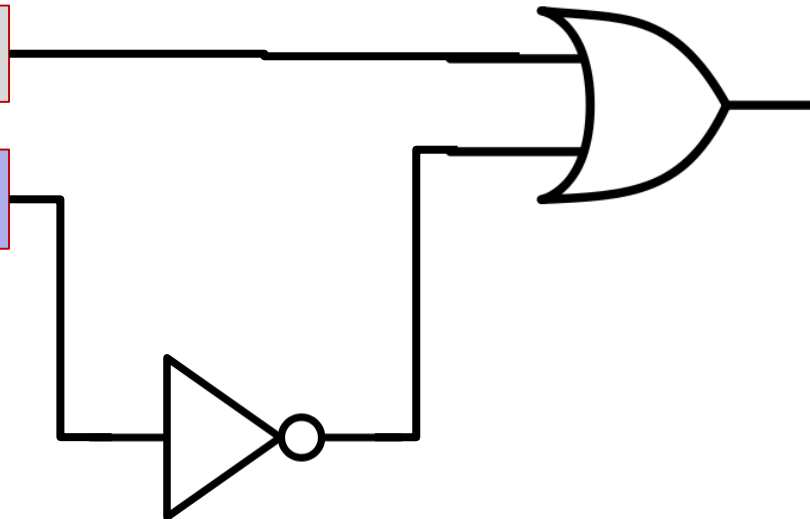

Switch	LDR	Street light
On	Dark	On
On	Bright	On
Off	Dark	On
Off	Bright	Off

Logic Gates


- Fire alarm security system

Hot=1, Cold=0

Heat Detector

Smoke Detector

Smoke=1, No smoke=0

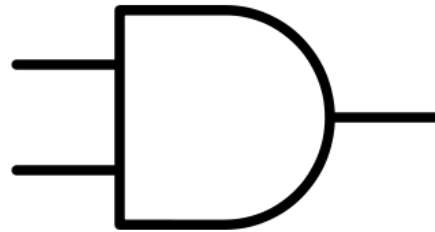

ON/OFF

Siren

Exercise: The system shown is not functioning well. Suggest a modification in order to make the system works.

Outline

- Boolean Logic
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- **Boolean Expressions**
- Logic Gates
- Logic Circuits
- Summary

Boolean Expressions

- Basic operations:

$C = A.B$ is read “C is equal to A and B.”

$z = x + y$ is read “z is equal to x OR y.”

$D = \bar{A}$ is read “D is equal to NOT A.”

- Using the basic operations, we can form more complex expressions:

$$Z = (A.B + C) + \bar{X}.Y$$

If $A=True, B=False, C=True, X=True, Y=False.$

$Z=(True.False+True)+False.False$

$=(False+True)+False=True+False=True$

Boolean Expressions

- Example

Assuming that $x=-10$, $y=50$, and $z=60$ determine the value of the following Boolean expression:

$$(0 < x < 50) \text{AND} (50 < y < 100) \text{OR} ([y-x]=z)$$

$$(0 < x < 50) \Rightarrow (0 < [-10] < 50) \Rightarrow \text{FALSE}$$

$$(50 < y < 100) \Rightarrow (50 < 50 < 100) \Rightarrow \text{FALSE}$$


$$([50 - (-10)] = 60) \Rightarrow (60 = 60) \Rightarrow \text{TRUE}$$

$$\text{FALSE AND FALSE} \Rightarrow \text{FALSE}$$

$$\text{FALSE OR TRUE} \Rightarrow \text{TRUE}$$


Boolean Expressions: Operator Precedence

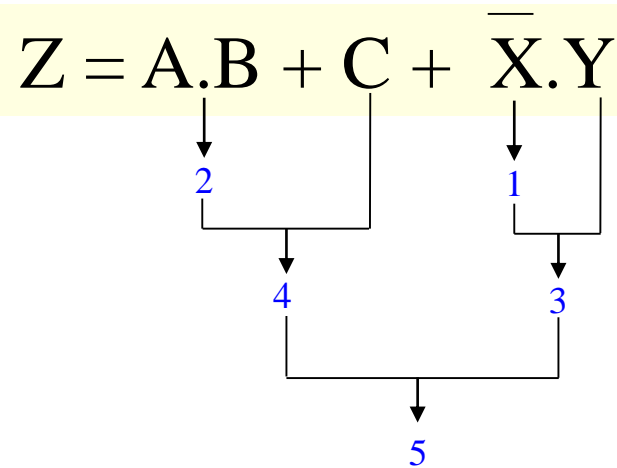- NOT has the highest precedence, followed by AND, and then OR.
- All higher-precedence operators are evaluated before any lower-precedence operators.
- Operators at the same precedence are evaluated left-to-right.



Boolean Expressions: Operator Precedence

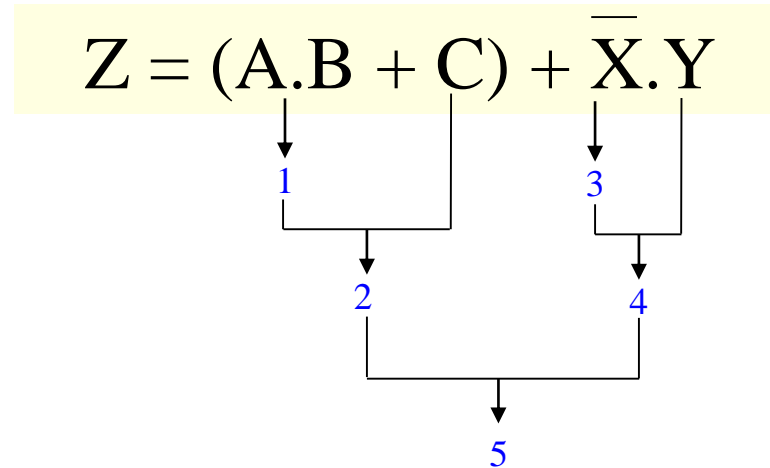- Parentheses can be used to override operator precedence.



Boolean Expressions: Truth Table

- A truth table represents all possible values of an expression given the possible values of its inputs.
- **How do we build a truth table?**
 - Step 1: Create columns for all variables
 - Step 2: Determine the number of rows needed (how many rows should appear?) \Rightarrow For n inputs, # of rows is 2^n .
 - Step 3: Define all possible values for the inputs starting from all 0's to all 1's, e.g. for 3 input variables from 000 to 111
 - Step 4: Find the value of the expression for each input value and fill in the table.

Boolean Expressions: Truth Table

Example: Boolean expression $F = X + Y.Z$

Inputs: X, Y, Z

Outputs: F

of inputs= $n=3$

of columns=#of inputs + #of outputs=4

of rows= $2^n=2^3=8$

Truth Table


Inputs			Output
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Outline


- Boolean Logic
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- **Logic Gates**
- Logic Circuits
- Summary

Logic Gates

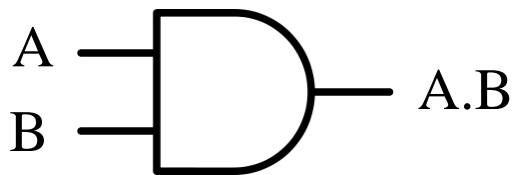
- A logic gates is an electronic device that operates on a collection of binary inputs to produce a binary output.
- The three basic logic gates are: AND gate, OR gate, NOT gate.



AND gate

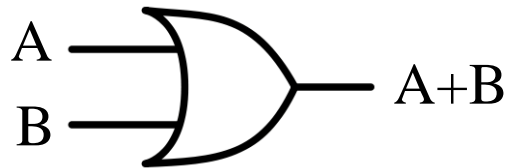


OR gate

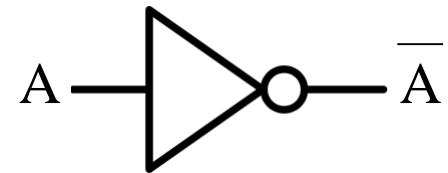

NOT gate

Logic Gates: AND Gate

- AND (product) of two inputs.

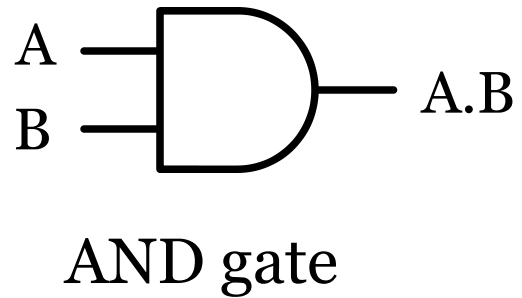


Truth Table

Inputs		Output
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

Logic Gates: OR Gate

- OR (sum) of two inputs.

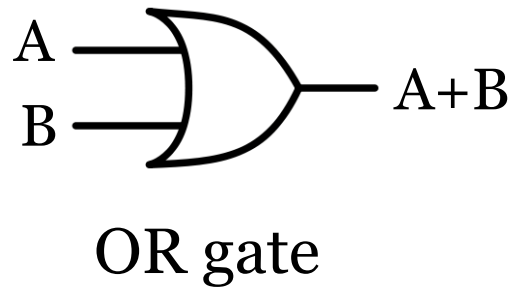


Truth Table

Inputs		Output
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

Logic Gates: NOT Gate

- NOT (complement) of one input.

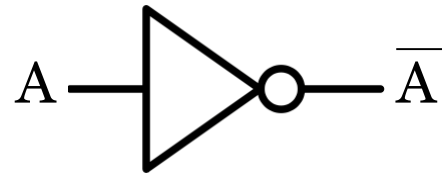

NOT gate

Truth Table

Input	Output
A	\bar{A}
0	1
1	0

Outline

- Boolean Logic
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- **Logic Circuits**
- Summary


Logic Circuits

- A circuit is a collection of logic gates that implements one or more Boolean expressions.

Example-1: Boolean expression $F = X + \bar{Y}.Z$

Inputs: X, Y, Z

Outputs: F

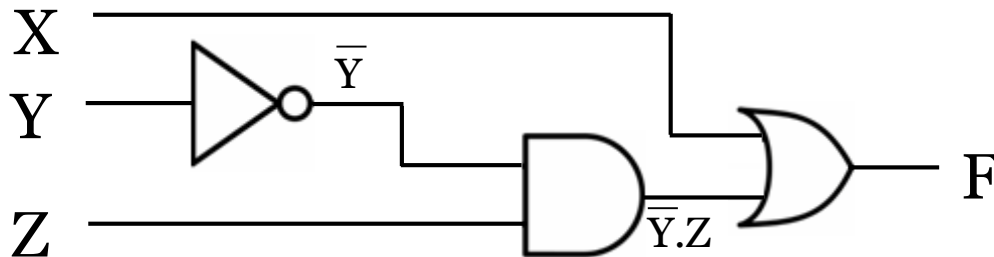

Logic Circuit

Truth Table

Inputs			Output
X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Logic Circuits

Example-2: Boolean expressions


$$S = \bar{X}.Y + X.\bar{Y}$$

$$C = X.Y$$

Inputs: X, Y Outputs: S, C

Truth Table


Inputs		Outputs	
X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

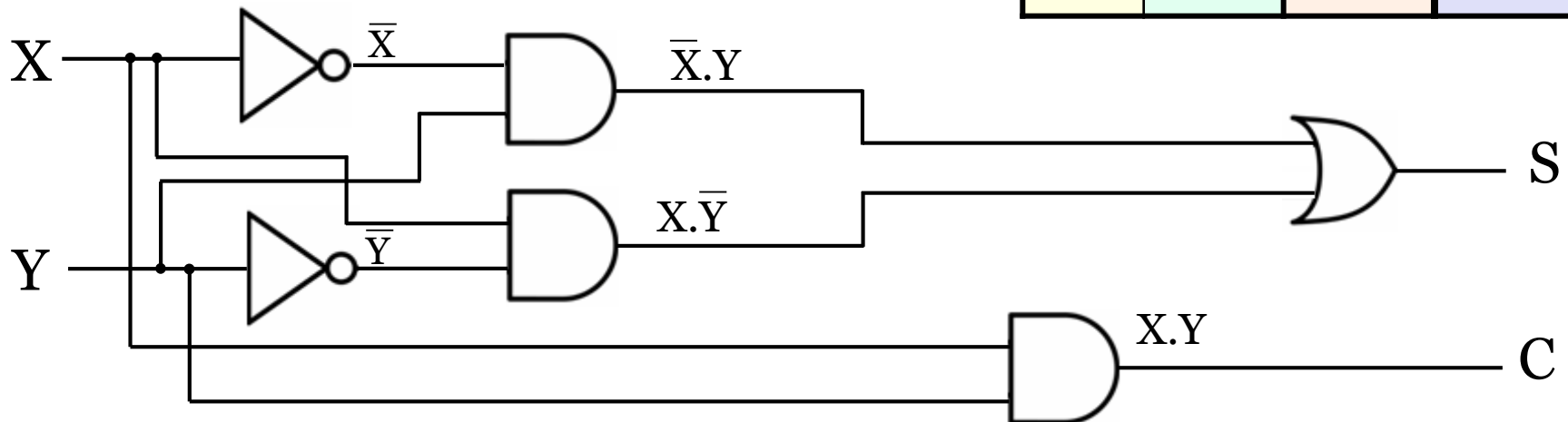

Logic Circuit - Half Adder

Logic Circuits

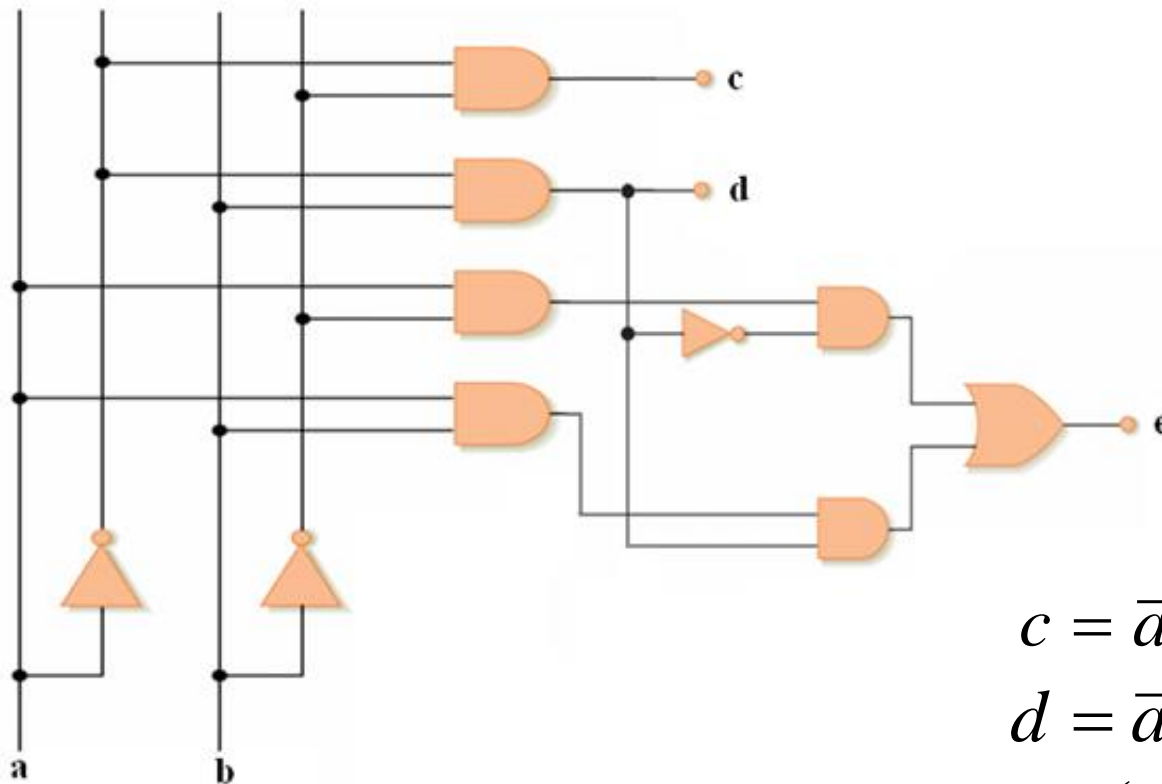Example-3: Determine the Boolean expression of the following circuit and construct the corresponding truth table considering that a and b are the input signals.



$$c = \bar{a}.\bar{b}$$

$$d = \bar{a}.b$$

$$e = (a.\bar{b}).\bar{d} + (a.b).d$$

Outline

- Boolean Logic
- Boolean Algebra
- Binary Variables
- Binary Operators
 - Logical AND
 - Logical OR
 - Logical Negation
- Boolean Expressions
- Logic Gates
- Logic Circuits
- **Summary**

Summary

- Boolean Algebra is a mathematical tool used in the analysis and design of digital circuits.
- OR, AND, NOT: basic Boolean operations.
- OR: HIGH output when any input is HIGH.
- AND: HIGH output only when all inputs are HIGH.
- NOT: output is the opposite logic level as the input.
- The order of evaluation in Boolean Expressions is: Parentheses, NOT, AND, OR.
- A logic gates is an electronic device that operates on a collection of binary inputs to produce a binary output.